


Testing Digital Systems I

Lecture 9: Boolean Testing Using Fault Models (D-Algorithm, PODEM)


Instructor: M. Tahoori

Copyright 2011, M. Tahoori TDS I: Lecture 9 1




D Algorithm (More Examples)

Copyright 2011, M. Tahoori TDS I: Lecture 9 2




Example: A/0

- Step 1
 - D-Drive: Set A = 1

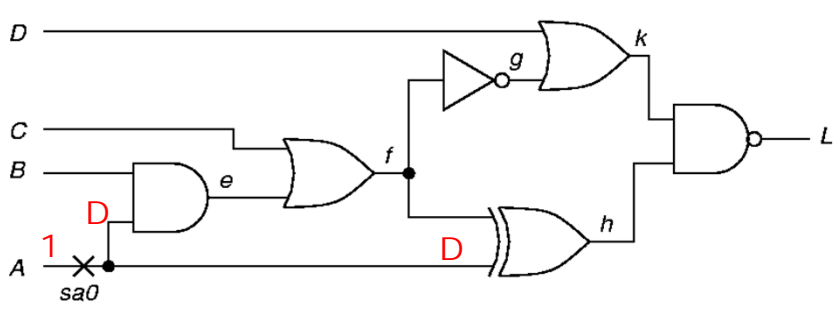


Copyright 2011, M. Tahoori TDS I: Lecture 9 3




Example: A/0

- Step 2
 - D-Drive : Set f = 0

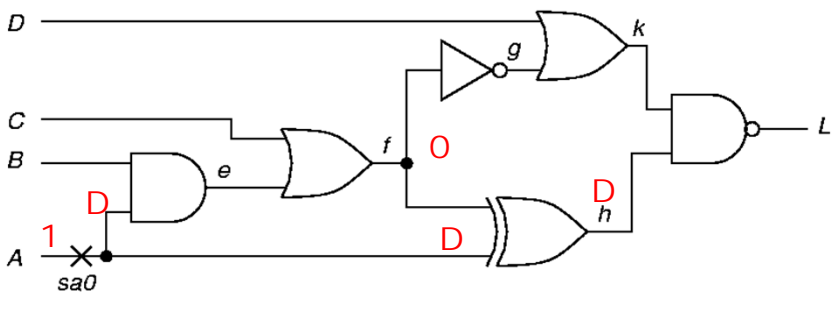


Copyright 2011, M. Tahoori TDS I: Lecture 9 4




Example: A/0

- Step 3
 - D-Drive : Set $k = 1$

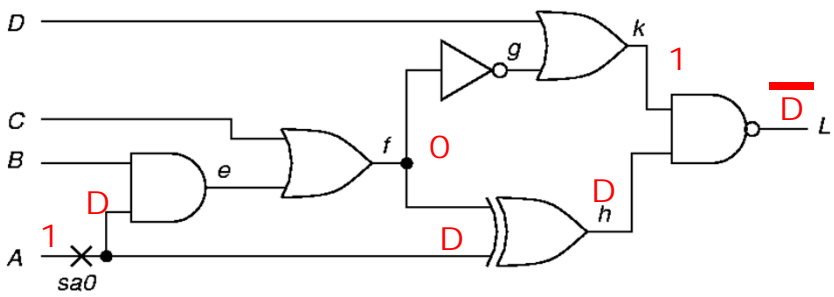


Copyright 2011, M. Tahoori TDS I: Lecture 9 5



Example: A/0

- Step 4
 - Consistency: Set $g = 1$

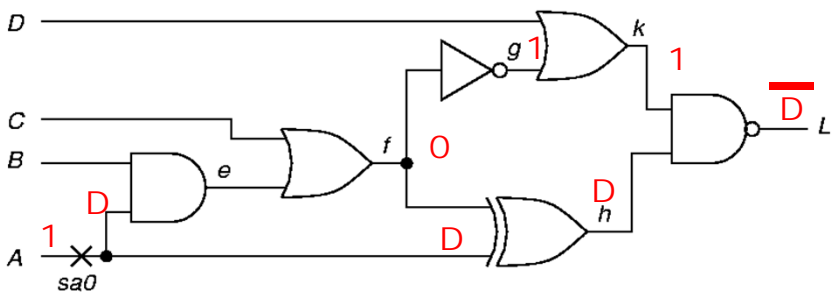


Copyright 2011, M. Tahoori TDS I: Lecture 9 6



Example: A/0

Step 5

- Consistency: $f = 0$
 - Already set

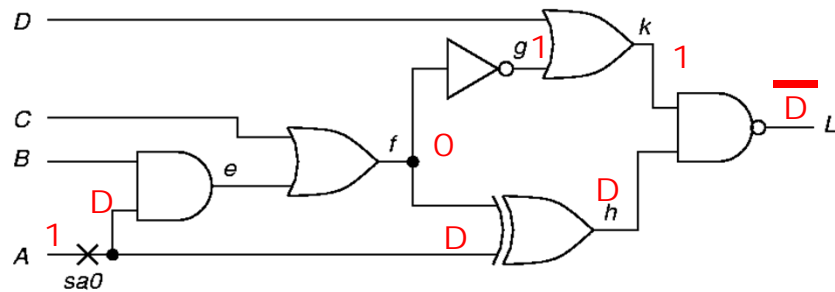

Copyright 2011, M. Tahoori

TDS I: Lecture 9


7



Example: A/0

Step 6

- Consistency: Set $c = 0$, Set $e = 0$

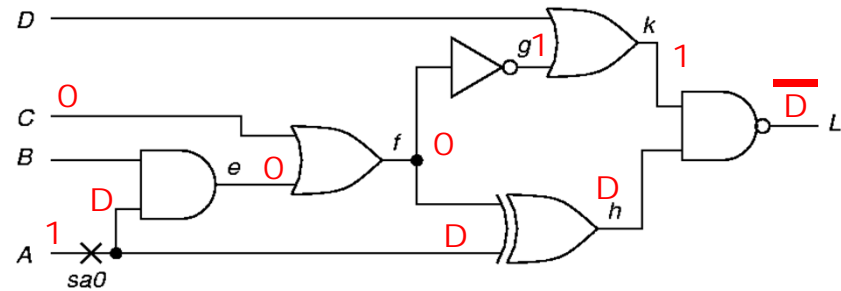

Copyright 2011, M. Tahoori


TDS I: Lecture 9

8



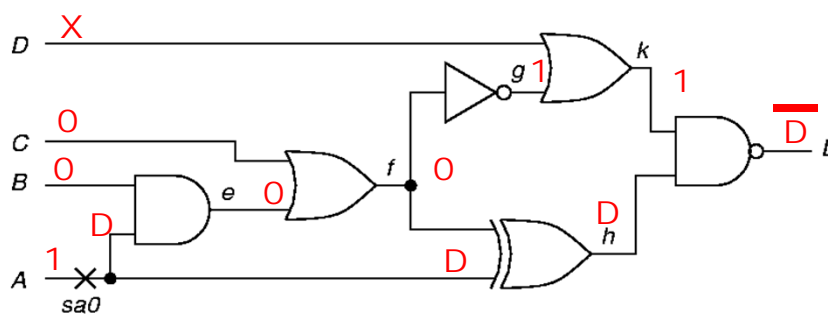Example: A/0

- Step 7
 - Consistency: Set $B = 0$
- Test found: $ABCD = 100X$



Copyright 2011, M. Tahoori


TDS I: Lecture 9

9



Example s/1

- Primitive D-cube of Failure

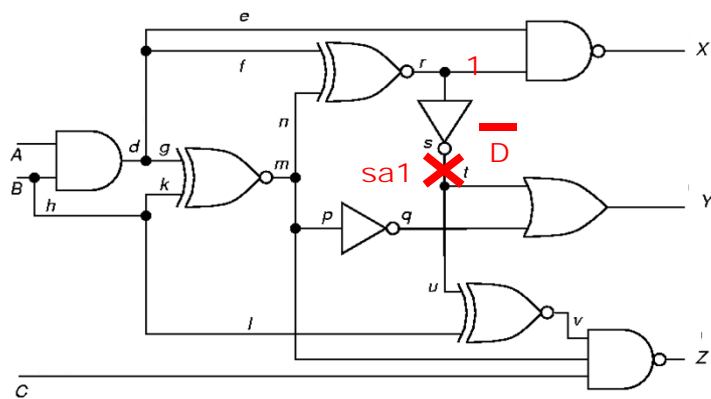

Copyright 2011, M. Tahoori


TDS I: Lecture 9

10



Example s/1

- Propagation D-cube for v

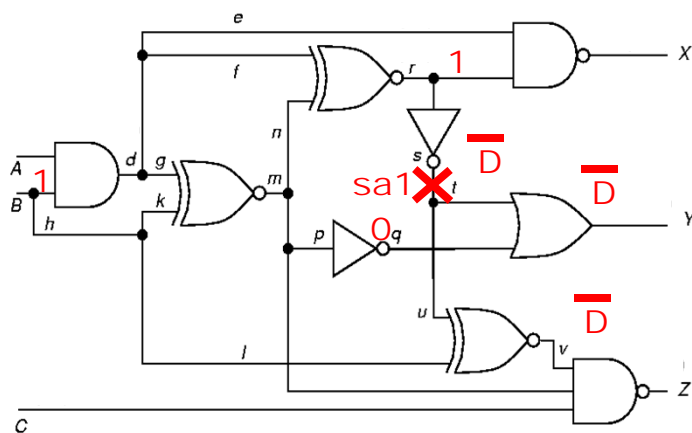

Copyright 2011, M. Tahoori


TDS I: Lecture 9

11



Example s/1

- Forward & Backward Implications

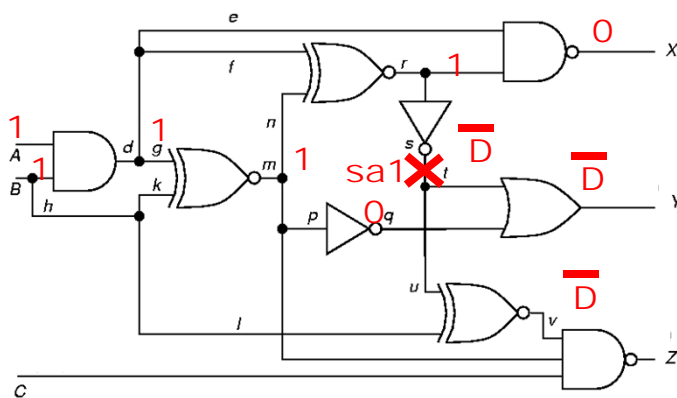

Copyright 2011, M. Tahoori


TDS I: Lecture 9

12



Example s/1

- Propagation D-cube for Z
- test found!

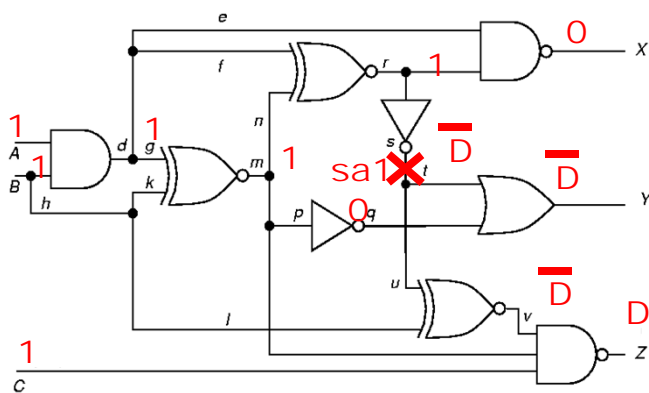

Copyright 2011, M. Tahoori


TDS I: Lecture 9

13



Example: u/1

- Primitive D-cube of Failure

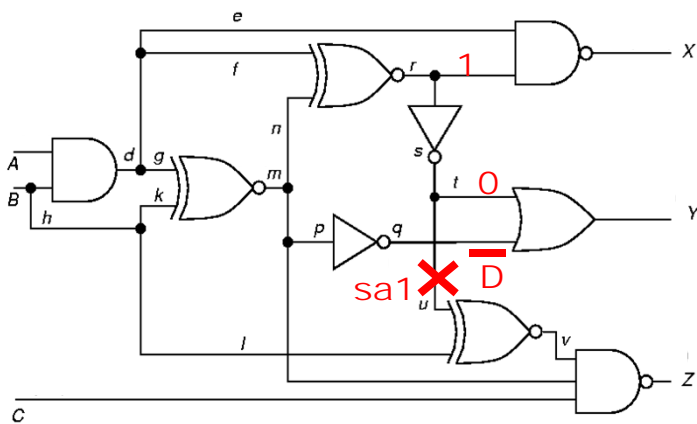

Copyright 2011, M. Tahoori


TDS I: Lecture 9

14



Example: u/1

- Propagation D-cube for v

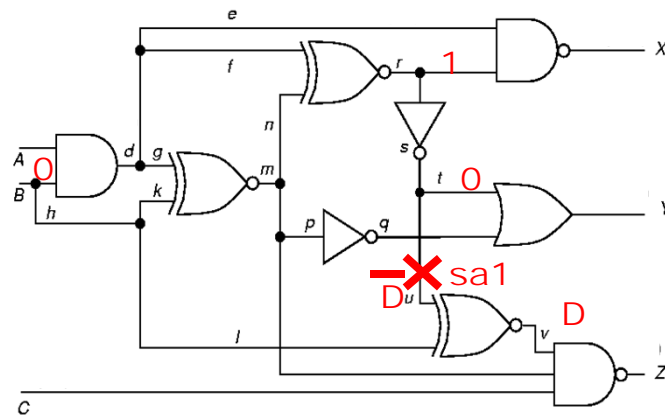

Copyright 2011, M. Tahoori


TDS I: Lecture 9

15



Example: u/1

- Forward and backward implications

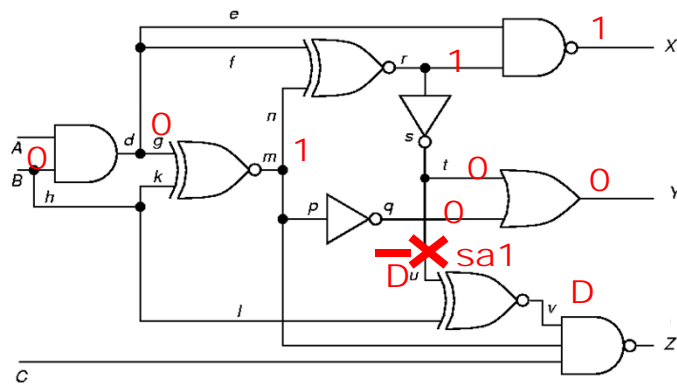

Copyright 2011, M. Tahoori

TDS I: Lecture 9

16



Example: u/1

- Inconsistency
 - $d = 0$ and $m = 1$
 - cannot justify $r = 1$ (equivalence)
- Backtrack
 - Remove $B = 0$ assignment

Copyright 2011, M. Tahoori


TDS I: Lecture 9

17



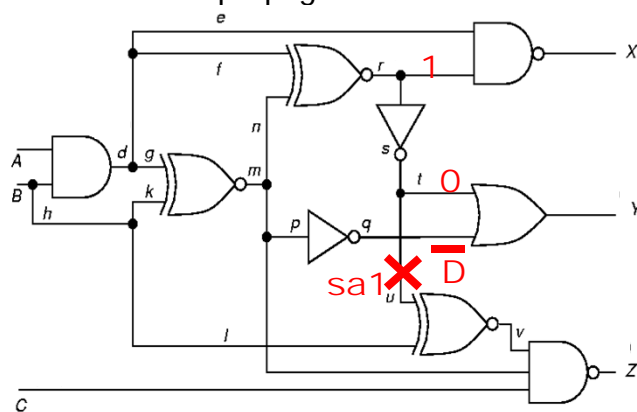Example: u/1

- Backtrack
 - Need alternate propagation D-cube for v



Copyright 2011, M. Tahoori


TDS I: Lecture 9

18



Example: u/1

- Propagation D-cube for v

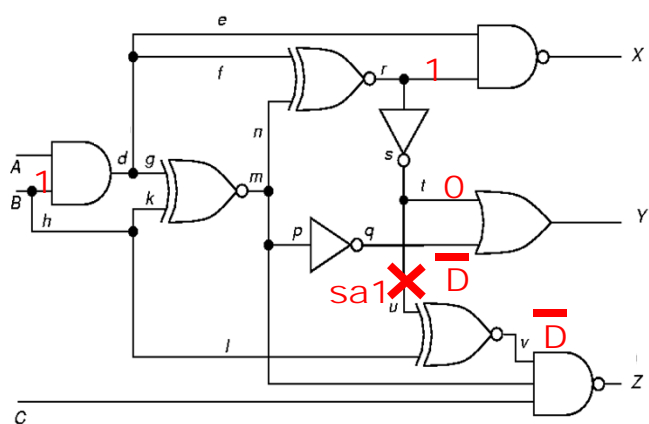

Copyright 2011, M. Tahoori


TDS I: Lecture 9

19



Example: u/1

- Propagation D-cube for Z

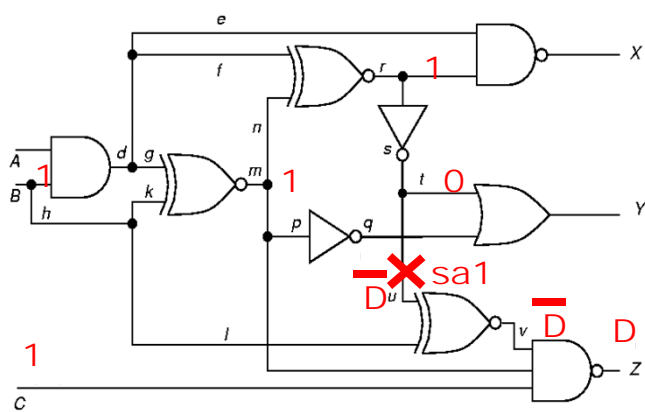

Copyright 2011, M. Tahoori


TDS I: Lecture 9

20



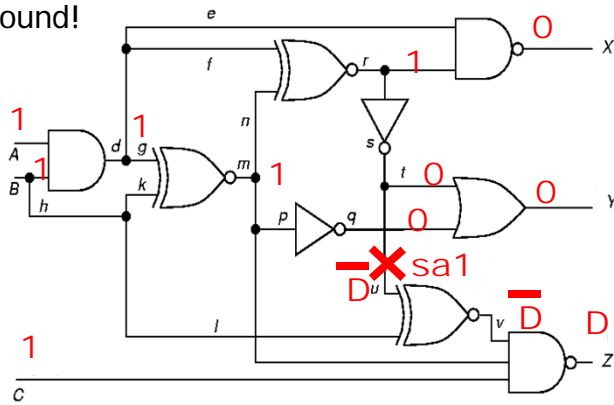Example: u/1

- Propagation D-cube for Z
- Implications
- Test Found!



Copyright 2011, M. Tahoori

TDS I: Lecture 9

21



PODEM

Copyright 2011, M. Tahoori

TDS I: Lecture 9

22



Motivation

- IBM introduced semiconductor DRAM memory into its mainframes – late 1970's
- Memory had error correction and translation circuits
 - To improved reliability
- D-ALG failed to generate test for these circuits
 - Search too undirected
 - Large XOR-gate trees
 - Must set all external inputs to define output
- Needed a better ATPG tool

Copyright 2011, M. Tahoori

TDS I: Lecture 9

23



PODEM -- Goel IBM (1981)

- Path Oriented DEcision Making
- New concepts introduced:
 - Expand binary decision tree only around primary inputs
 - This reduced size of tree from 2^n to $2^{\text{num_PI}}$
 - Use X-PATH-CHECK
 - To test whether D-frontier still there
 - D-Algorithm tends to continue intersecting D-Cubes
 - Even when D-Frontier disappeared
 - Objectives
 - bring ATPG closer to propagating D (\bar{D}) to PO
 - Backtracing
 - To obtain a PI assignment given an initial objective

Copyright 2011, M. Tahoori

TDS I: Lecture 9

24



Assigning Input Values (PODEM)

1. Assign value to an unassigned primary input
2. Determine all implications of assignment
3. If test is generated, exit; else
4. Is test is possible with additional input assignments ?
 - fault site doesn't have fault value assigned
 - Path of unassigned leads from D (\bar{D}) to an output
 - If yes, go to 1, if no
5. Change input assignments to untried combination, go to 2
 - If no untried combination exists — untestable fault

Copyright 2011, M. Tahoori


TDS I: Lecture 9

25



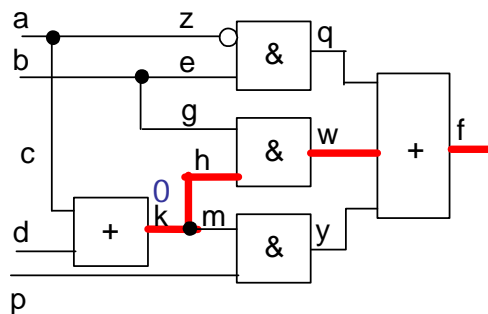Example: Test For k/1

- Put D' on k
 - D-Alg: assigned a D' to k and propagate it to output f
 - PODEM: try to justify 0 on k



Copyright 2011, M. Tahoori


TDS I: Lecture 9

26



Example: Test For k/1

- Justify 0 on d
- Implication

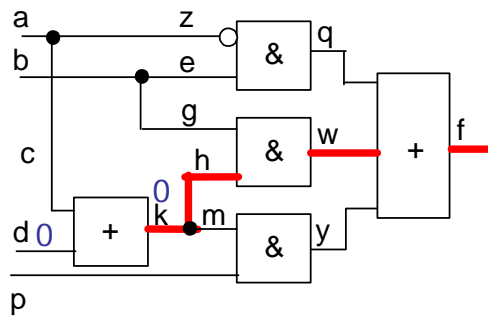

Copyright 2011, M. Tahoori


TDS I: Lecture 9

27



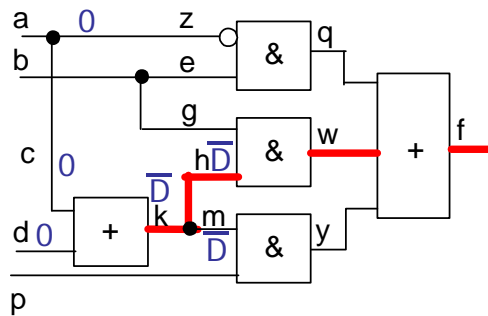Example: Test For k/1


- K still hasn't D'
- Justify 0 on c
- Implication: $k=h=m=D'$



Copyright 2011, M. Tahoori


TDS I: Lecture 9

28



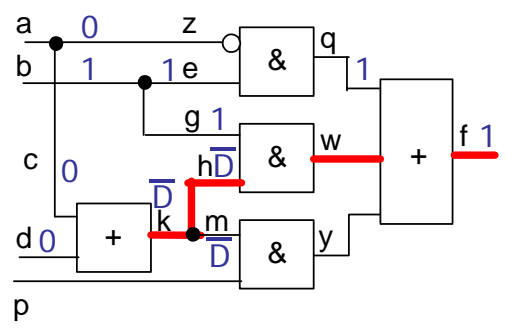
Example: Test For k/1

- Propagate through w
- Set $g = 1$
- Implication




Copyright 2011, M. Tahoori TDS I: Lecture 9 29



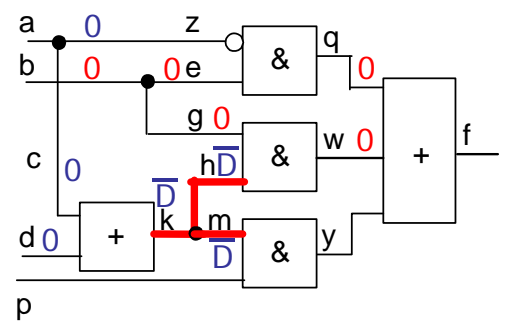
Example: Test For k/1

- Conflict
 - f is 1 so propagation is blocked
- Reverse the last assignment made to a PI
 - Set $b = 0$
- Implication




Copyright 2011, M. Tahoori TDS I: Lecture 9 30



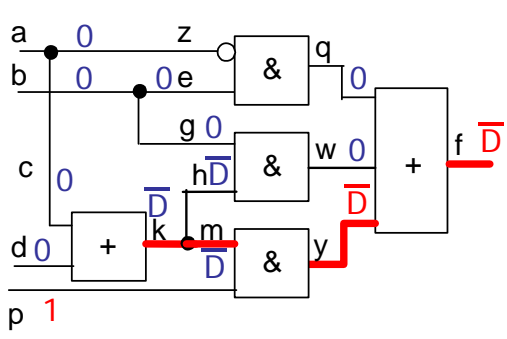
Example: Test For k/1

- There is a propagation path from m to f
 - Set $p = 1$
- Implication
- Test found
 - $abcd = 0001$



Copyright 2011, M. Tahoori
TDS I: Lecture 9
31




Another Example

Copyright 2011, M. Tahoori
TDS I: Lecture 9
32



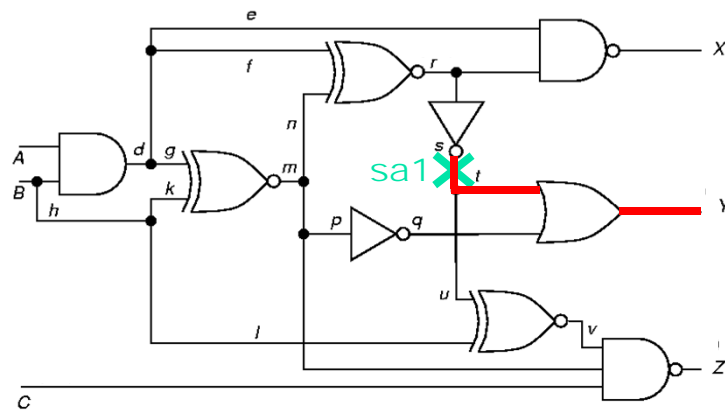Example: S/1

- Select path s – Y for fault propagation



Copyright 2011, M. Tahoori


TDS I: Lecture 9

33



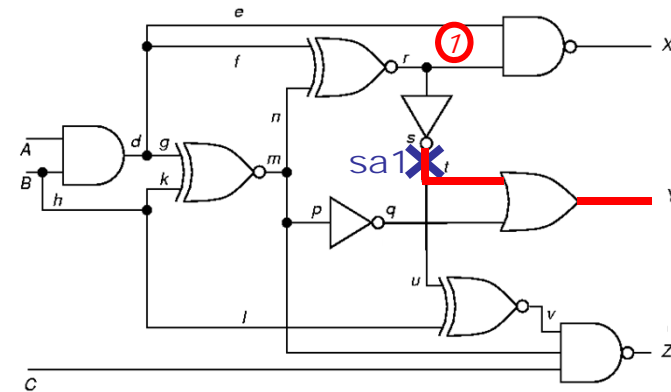Example: S/1

- Initial objective:
 - Set r to 1 to sensitize fault



Copyright 2011, M. Tahoori


TDS I: Lecture 9

34



Example: S/1

- Backtrace from r

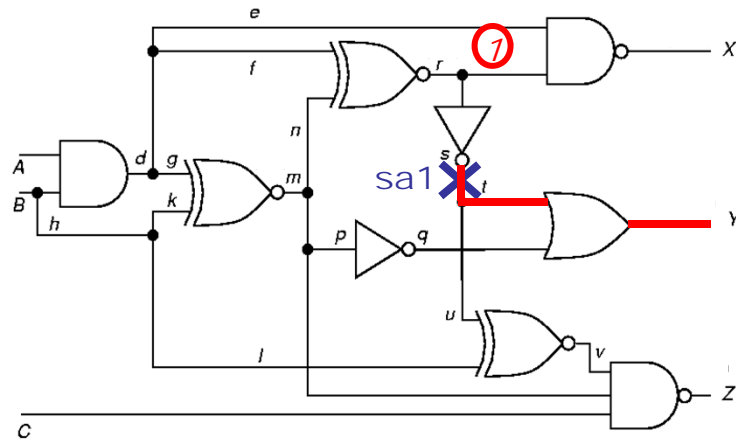

Copyright 2011, M. Tahoori


TDS I: Lecture 9

35



Example: S/1


- Set A = 0 in implication stack

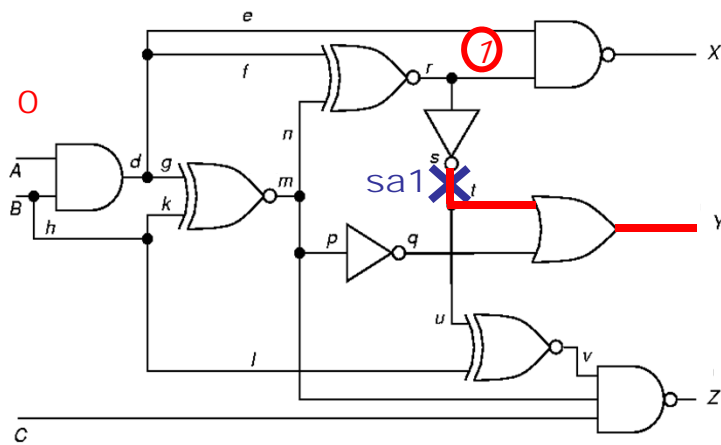

Copyright 2011, M. Tahoori


TDS I: Lecture 9

36




Example: S/1

- Forward implications: $d = 0, X = 1$

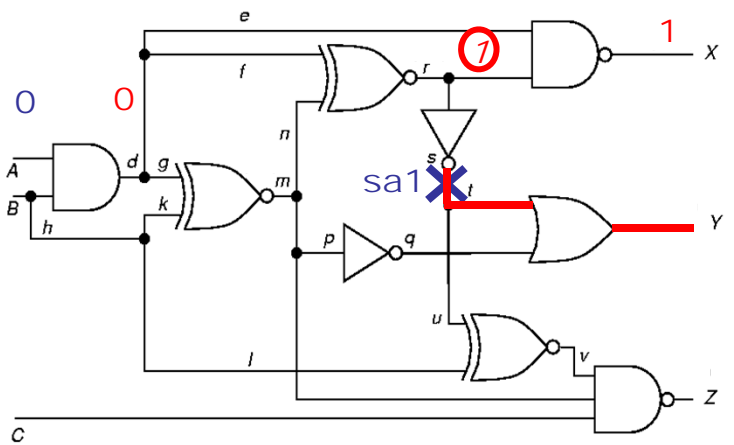


Copyright 2011, M. Tahoori TDS I: Lecture 9 37




Example: S/1

- Initial objective: set r to 1

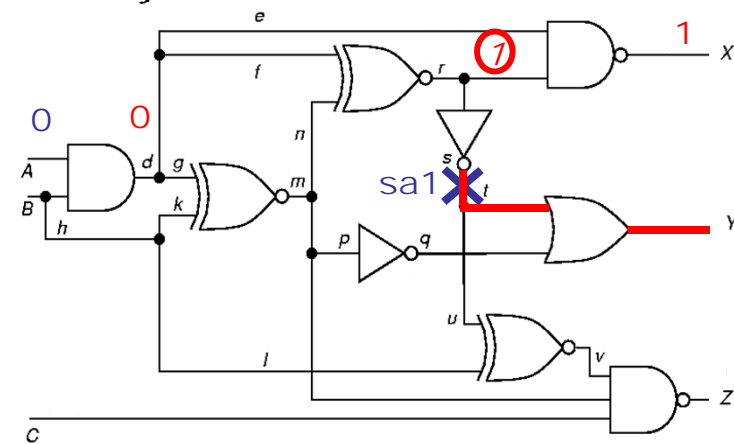


Copyright 2011, M. Tahoori TDS I: Lecture 9 38



Example: S/1


- Backtrace from r again

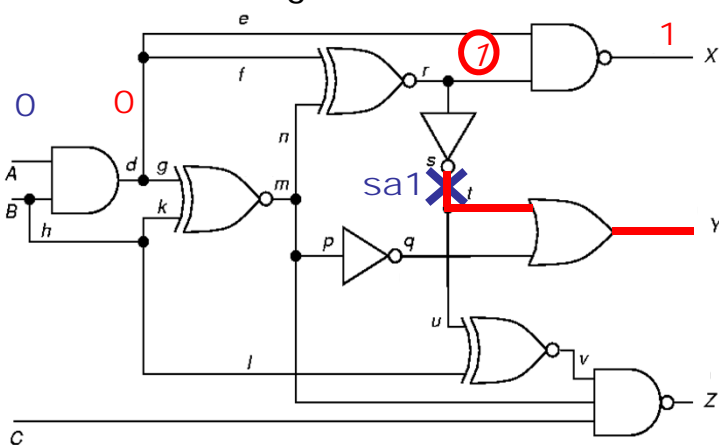

Copyright 2011, M. Tahoori


TDS I: Lecture 9

39



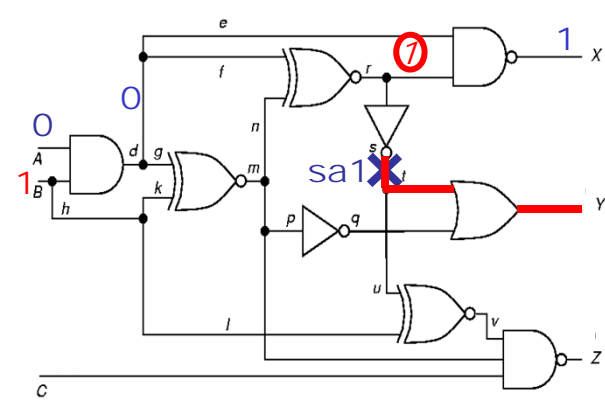Example: S/1

- Set B to 1.
 - Implications in stack: A = 0, B = 1



Copyright 2011, M. Tahoori


TDS I: Lecture 9

40



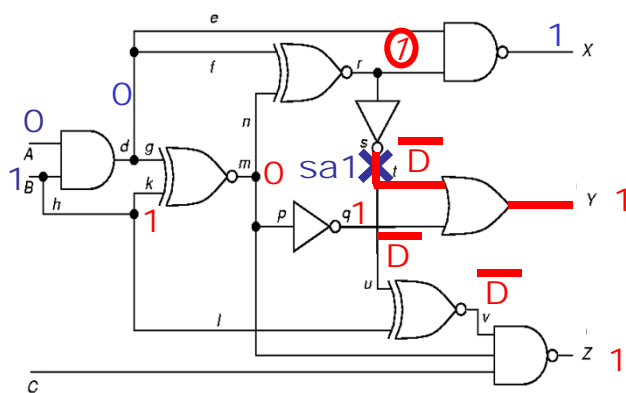Example: S/1

- Forward implications:
- $k = 1, m = 0, r = 1, q = 1, Y = 1, s = \overline{D}, u = \overline{D}, v = \overline{D}, Z = 1$



Copyright 2011, M. Tahoori


TDS I: Lecture 9

41



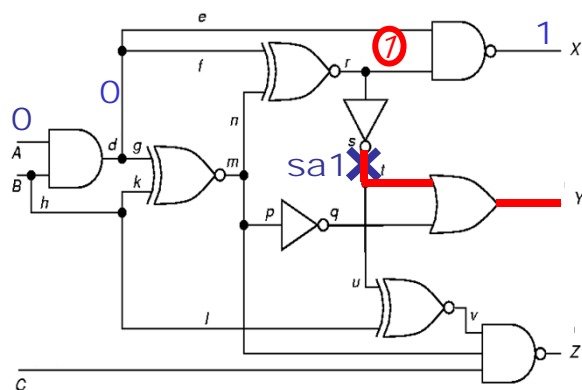Example: S/1

- X-PATH-CHECK
- paths $s - Y$ and $s - u - v - Z$ blocked



Copyright 2011, M. Tahoori


TDS I: Lecture 9

42



Example: S/1

- Set B = 0 (alternate assignment)

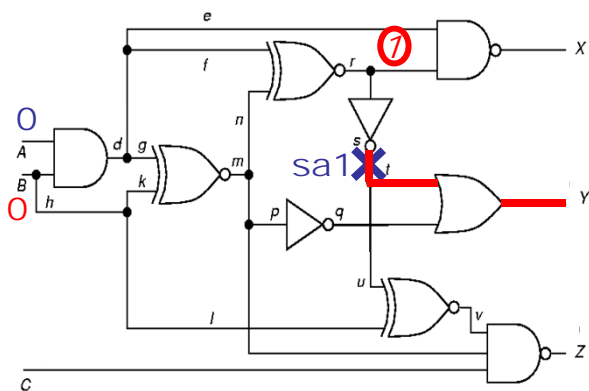

Copyright 2011, M. Tahoori


TDS I: Lecture 9

43



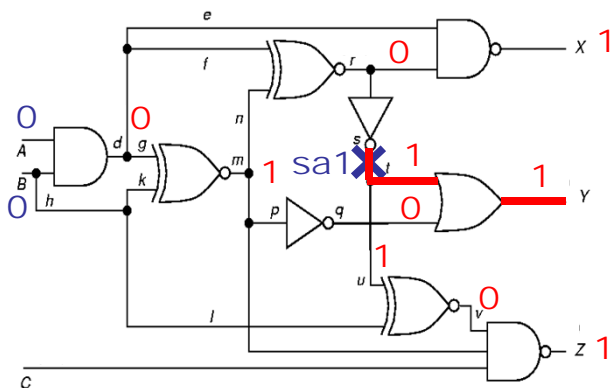Example: S/1

- Forward implications:
- $d = 0, X = 1, m = 1, r = 0, s = 1, q = 0, Y = 1, v = 0, Z = 1$
- Fault not sensitized



Copyright 2011, M. Tahoori


TDS I: Lecture 9

44



Example: S/1

- Set A = 1 (alternate assignment)

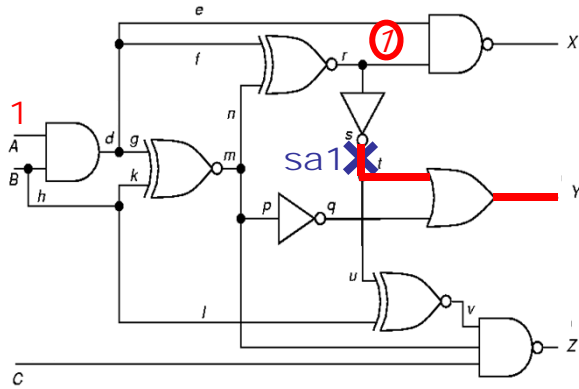

Copyright 2011, M. Tahoori


TDS I: Lecture 9

45



Example: S/1

- Backtrace from r again

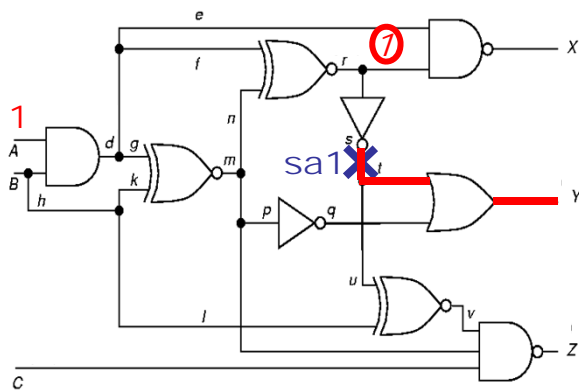

Copyright 2011, M. Tahoori


TDS I: Lecture 9

46



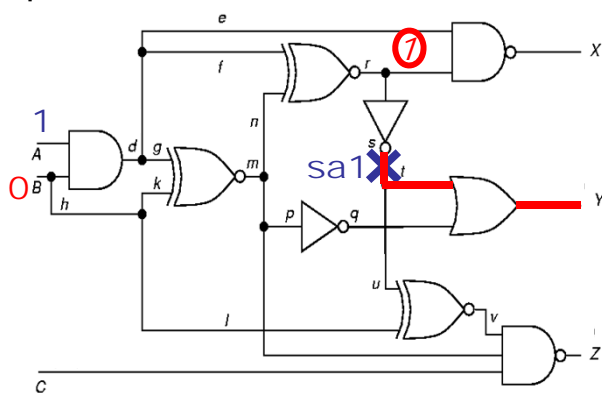Example: S/1

- Set $B = 0$.
- Implications in stack: $A = 1, B = 0$



Copyright 2011, M. Tahoori


TDS I: Lecture 9

47



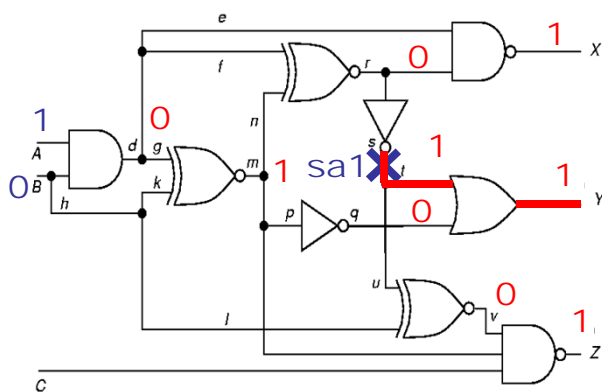Example: S/1

- Forward implications:
 - $d = 0, X = 1, m = 1, r = 0$.
- Conflict: fault not sensitized. Backtrack



Copyright 2011, M. Tahoori


TDS I: Lecture 9

48



Example: S/1

- Set $B = 1$ (alternative assignment)

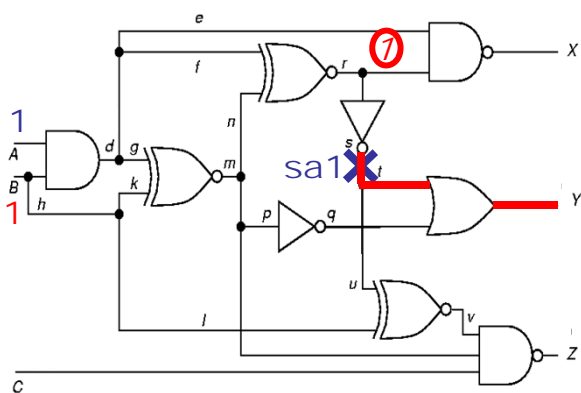

Copyright 2011, M. Tahoori


TDS I: Lecture 9

49



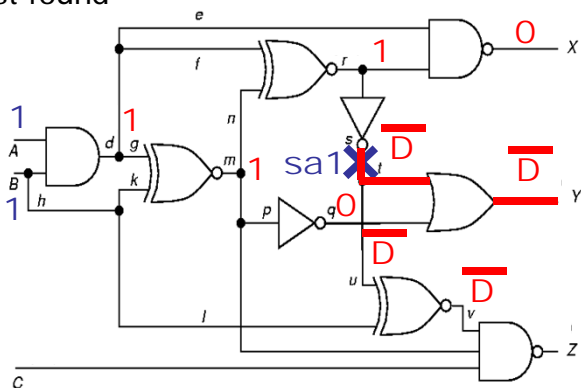Example: S/1

- Forward implications:
 - $d = 1, m = 1, r = 1, q = 0, s = \overline{D}, v = \overline{D}, X = 0, Y = \overline{D}$
- Test found



Copyright 2011, M. Tahoori

TDS I: Lecture 9

50



PODEM

- Major aspects
 - Which primary input should be assigned a logic value?
 - What value to assign to the selected primary input?
 - Determining inconsistencies in primary input assignments
 - Handling inconsistencies



Which PI to Choose?

- Decision gate
 - Logic value at the output of a gate is such that only one input of the gate can control its output to the desired value
 - AND with output 0
- Imply gate
 - Logic value at the output of a gate is such that all inputs of the gate must be at a particular value in order to control its output to the desired value
 - AND with output 1
- To justify a logic value at the output of a decision gate, choose the "easiest" input.
 - The shortest logical path to primary inputs or has the best controllability
- To justify a logic value at the output of an imply gate, choose the "hardest" input
 - The longest logical path to primary inputs or has the worst controllability



What Value to Assign?

- Path from the objective site to the selected primary input has an **even** number of inversions
 - Assign the same value to PI as the objective
- Path from the objective site to the selected primary input has an **odd** number of inversions
 - Assign the opposite value of the objective to PI

Copyright 2011, M. Tahoori

TDS I: Lecture 9

53



Inconsistencies in PI Assignment

- After every primary input assignment, an implication step is performed.
- During implication, inconsistencies in primary input assignments are detected using the following rules:
 - If there are conflicting assignments at the same signal line of the network
 - If the logic value at the fault site doesn't activate the fault
 - If there is no path from the fault site to a primary output such that all side inputs of that path are either X or set at non-controlling values

Copyright 2011, M. Tahoori

TDS I: Lecture 9

54



Handling Inconsistencies

- Backtracking
 - Flip the logic value at the primary input
 - Which was the last one to be assigned a value
 - Stack of primary inputs that have been assigned values
 - After flipping implication step is performed
 - No inconsistency detected
 - Continue
 - Otherwise
 - That primary input is removed from the stack and
 - X is assigned to that primary input
 - POP the next assigned PI from stack and repeat