


# Testing Digital Systems I

---

## Lecture 9: Boolean Testing Using Fault Models (D-Algorithm, PODEM)

Instructor: M. Tahoori

Copyright 2019, M. Tahoori      TDS I: Lecture 9      1



---

## D Algorithm (More Examples)

Copyright 2019, M. Tahoori      TDS I: Lecture 9      2

### Example: A/0

- Step 1
  - D-Drive: Set A = 1

Copyright 2019, M. Tahoori TDS I: Lecture 9 3

### Example: A/0

- Step 2
  - D-Drive : Set f = 0

Copyright 2019, M. Tahoori TDS I: Lecture 9 4

### Example: A/0

- Step 3
  - D-Drive : Set  $k = 1$

Copyright 2019, M. Tahoori TDS I: Lecture 9 5

### Example: A/0

- Step 4
  - Consistency: Set  $g = 1$

Copyright 2019, M. Tahoori TDS I: Lecture 9 6

### Example: A/0

- Step 5
  - Consistency:  $f = 0$ 
    - Already set

Copyright 2019, M. Tahoori TDS I: Lecture 9 7

### Example: A/0

- Step 6
  - Consistency: Set  $c = 0$ , Set  $e = 0$

Copyright 2019, M. Tahoori TDS I: Lecture 9 8

### Example: A/0

- Step 7
  - Consistency: Set  $B = 0$
- Test found:  $ABCD = 100X$

Copyright 2019, M. Tahoori TDS I: Lecture 9 9


### Example s/1

- Primitive D-cube of Failure

Copyright 2019, M. Tahoori TDS I: Lecture 9 10

## Example s/1

- Propagation D-cube for v

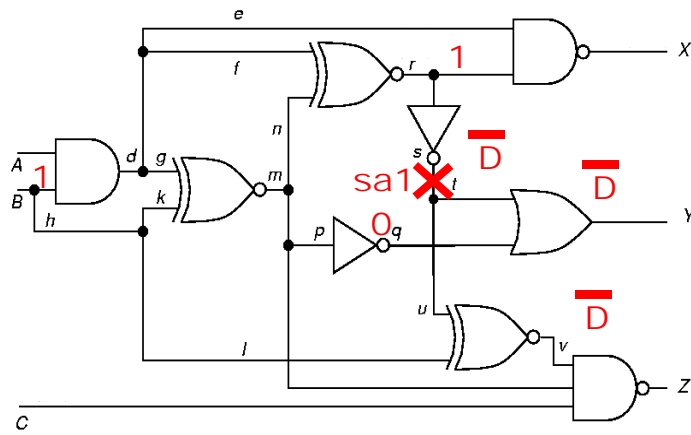


Copyright 2019, M. Tahoori

TDS I: Lecture 9

11

## Example s/1

- Forward & Backward Implications

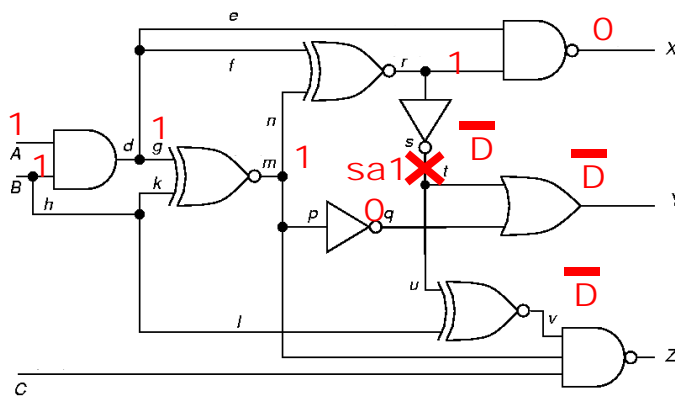


Copyright 2019, M. Tahoori

TDS I: Lecture 9

12

### Example s/1

- Propagation D-cube for Z
- test found!

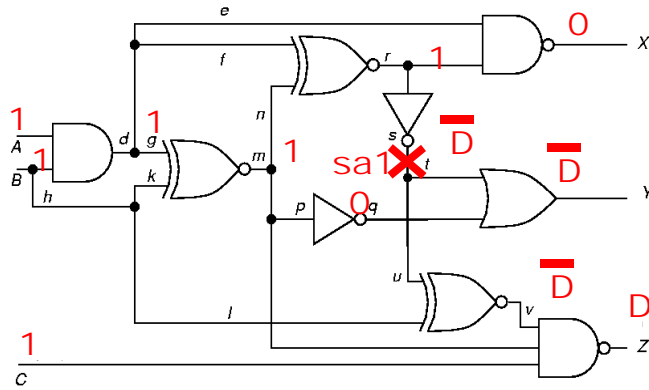


Copyright 2019, M. Tahoori

TDS I: Lecture 9

13

### Example: u/1

- Primitive D-cube of Failure

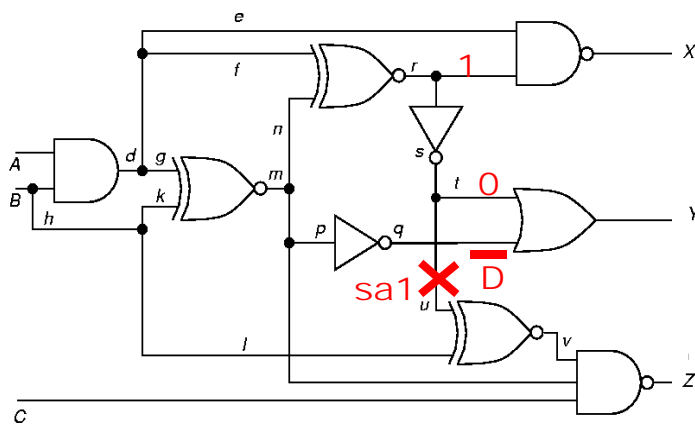

Copyright 2019, M. Tahoori


TDS I: Lecture 9

14



## Example: u/1

- Propagation D-cube for v

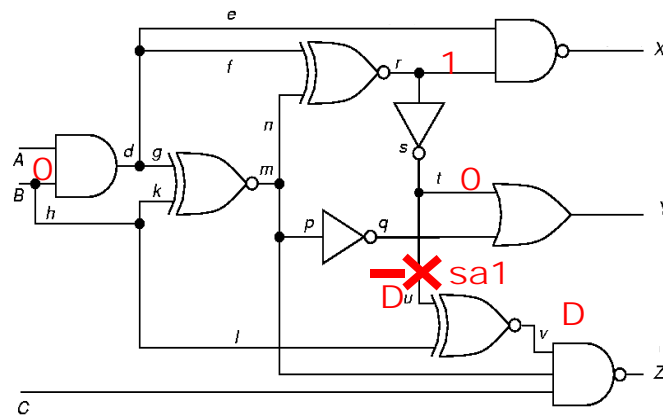

Copyright 2019, M. Tahoori


TDS I: Lecture 9

15



## Example: u/1

- Forward and backward implications

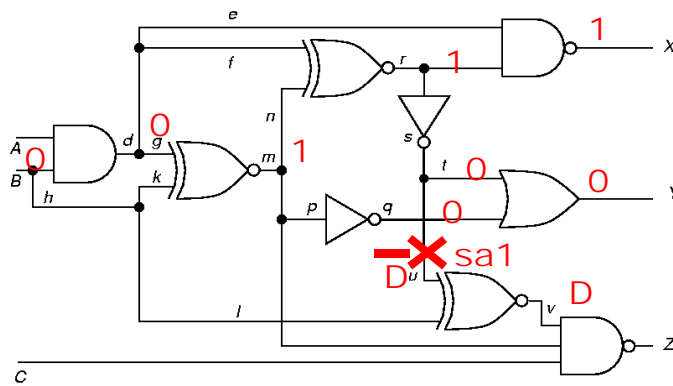

Copyright 2019, M. Tahoori

TDS I: Lecture 9

16



## Example: u/1

- Inconsistency
  - $d = 0$  and  $m = 1$ 
    - cannot justify  $r = 1$  (equivalence)
- Backtrack
  - Remove  $B = 0$  assignment


Copyright 2019, M. Tahoori

TDS I: Lecture 9

17
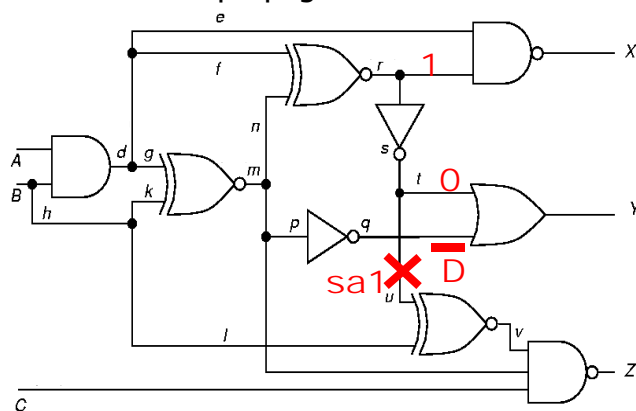
## Example: u/1

- Backtrack
  - Need alternate propagation D-cube for  $v$




Copyright 2019, M. Tahoori

TDS I: Lecture 9

18

**Example: u/1**

- Propagation D-cube for v

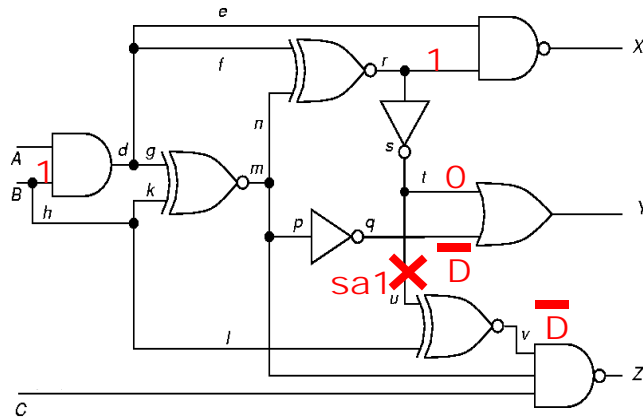


Copyright 2019, M. Tahoori

TDS I: Lecture 9

19

**Example: u/1**

- Propagation D-cube for Z

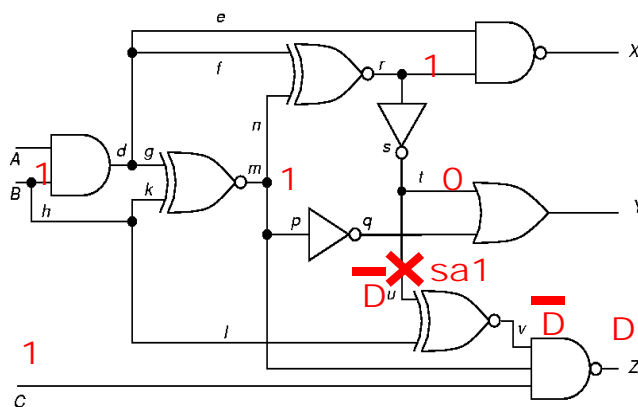

Copyright 2019, M. Tahoori

TDS I: Lecture 9

20

**Example: u/1**

- Propagation D-cube for Z
- Implications
- Test Found!

Copyright 2019, M. Tahoori      TDS I: Lecture 9      21

**PODEM**

Copyright 2019, M. Tahoori      TDS I: Lecture 9      22



## Motivation

- IBM introduced semiconductor DRAM memory into its mainframes – late 1970's
- Memory had error correction and translation circuits
  - To improved reliability
- D-ALG failed to generate test for these circuits
  - Search too undirected
  - Large XOR-gate trees
  - Must set all external inputs to define output
- Needed a better ATPG tool

Copyright 2019, M. Tahoori

TDS I: Lecture 9

23



## PODEM -- Goel IBM (1981)

- Path Oriented DEcision Making
- New concepts introduced:
  - Expand binary decision tree only around primary inputs
    - This reduced size of tree from  $2^n$  to  $2^{\text{num\_PI}}$
  - Use X-PATH-CHECK
    - To test whether D-frontier still there
    - D-Algorithm tends to continue intersecting D-Cubes
      - Even when D-Frontier disappeared
  - Objectives
    - bring ATPG closer to propagating D ( $\bar{D}$ ) to PO
  - Backtracing
    - To obtain a PI assignment given an initial objective

Copyright 2019, M. Tahoori

TDS I: Lecture 9

24

## Assigning Input Values ( PODEM)

1. Assign value to an unassigned primary input
2. Determine all implications of assignment
3. If test is generated, exit; else
4. Is test is possible with additional input assignments ?
  - fault site doesn't have fault value assigned
  - Path of unassigned leads from D ( $\bar{D}$ ) to an output
  - If yes, go to 1, if no
5. Change input assignments to untried combination, go to 2
  - If no untried combination exists — untestable fault

Copyright 2019, M. Tahoori TDS I: Lecture 9 25

## Example: Test For k/1

- Put D' on k
  - D-Alg: assigned a D' to k and propagate it to output f
  - PODEM: try to justify 0 on k

Copyright 2019, M. Tahoori TDS I: Lecture 9 26

### Example: Test For k/1

- Justify 0 on d
- Implication

Copyright 2019, M. Tahoori TDS I: Lecture 9 27

### Example: Test For k/1

- K still hasn't D'
- Justify 0 on c
- Implication:  $k=h=m=D'$

Copyright 2019, M. Tahoori TDS I: Lecture 9 28

### Example: Test For k/1

- Propagate through w
- Set  $g = 1$
- Implication

Copyright 2019, M. Tahoori      TDS I: Lecture 9      29

### Example: Test For k/1


- Conflict
  - $f$  is 1 so propagation is blocked
- Reverse the last assignment made to a PI
  - Set  $b = 0$
- Implication

Copyright 2019, M. Tahoori      TDS I: Lecture 9      30


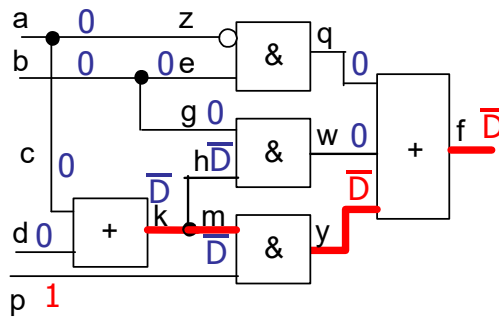
### Example: Test For k/1

- There is a propagation path from m to f
  - Set  $p = 1$
- Implication
- Test found
  - $abcd = 0001$




### Another Example




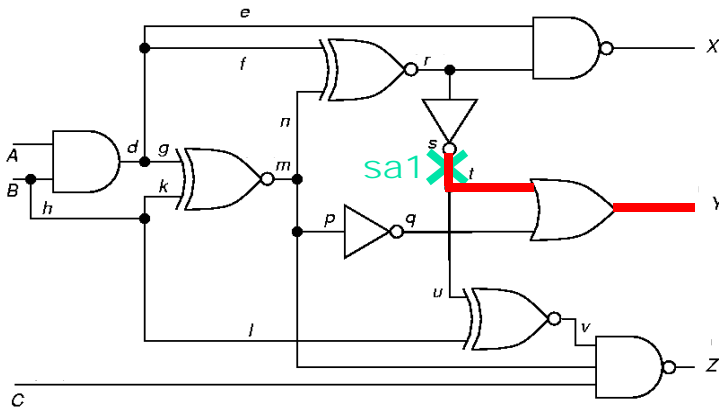
### Example: S/1

- Select path s – Y for fault propagation



Copyright 2019, M. Tahoori


TDS I: Lecture 9

33


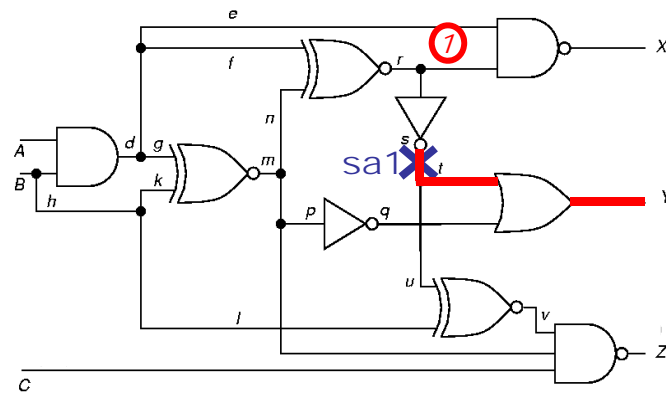
### Example: S/1

- Initial objective:
  - Set r to 1 to sensitize fault



Copyright 2019, M. Tahoori

TDS I: Lecture 9

34

### Example: S/1

- Backtrace from r

Copyright 2019, M. Tahoori TDS I: Lecture 9 35

### Example: S/1

- Set A = 0 in implication stack

Copyright 2019, M. Tahoori TDS I: Lecture 9 36

### Example: S/1

- Forward implications:  $d = 0, X = 1$

Copyright 2019, M. Tahoori TDS I: Lecture 9 37

### Example: S/1

- Initial objective: set  $r$  to 1

Copyright 2019, M. Tahoori TDS I: Lecture 9 38

### Example: S/1

- Backtrace from r again

Copyright 2019, M. Tahoori TDS I: Lecture 9 39

### Example: S/1

- Set B to 1.
  - Implications in stack: A = 0, B = 1

Copyright 2019, M. Tahoori TDS I: Lecture 9 40

### Example: S/1

- Forward implications:
- $k = 1, m = 0, r = 1, q = 1, Y = 1, s = \bar{D}, u = \bar{D}, v = \bar{D}, Z = 1$

Copyright 2019, M. Tahoori      TDS I: Lecture 9      41

### Example: S/1


- X-PATH-CHECK
- paths  $s - Y$  and  $s - u - v - Z$  blocked

Copyright 2019, M. Tahoori      TDS I: Lecture 9      42



## Example: S/1

- Set B = 0 (alternate assignment)

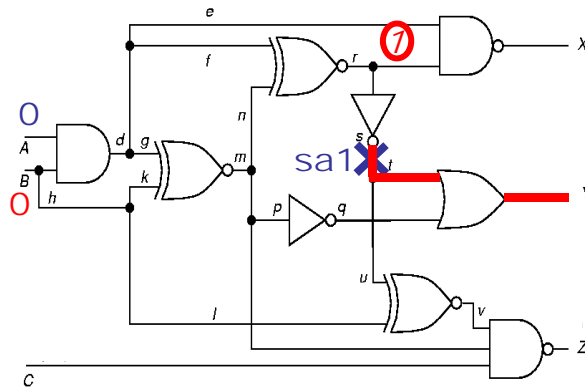

Copyright 2019, M. Tahoori


TDS I: Lecture 9

43


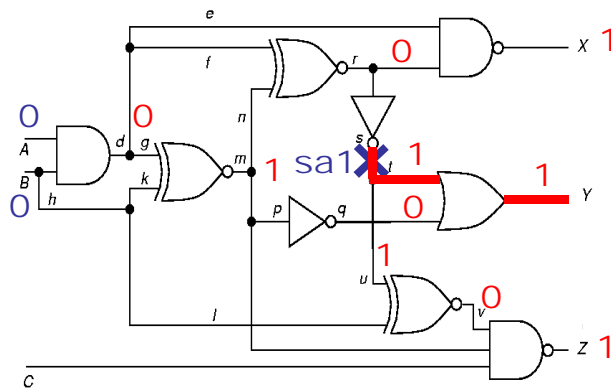
## Example: S/1

- Forward implications:
- d = 0, X=1, m = 1, r = 0, s = 1, q = 0, Y = 1, v = 0, Z = 1
- Fault not sensitized



Copyright 2019, M. Tahoori


TDS I: Lecture 9

44



## Example: S/1

- Set A = 1 (alternate assignment)

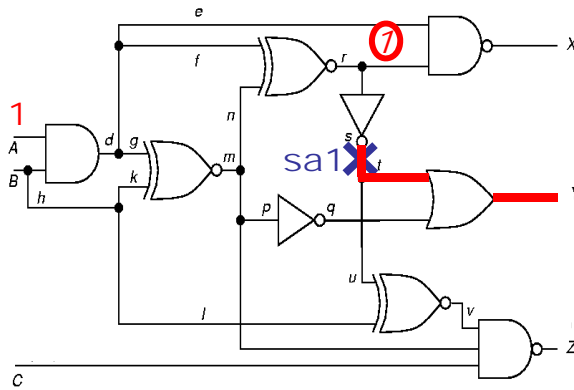

Copyright 2019, M. Tahoori


TDS I: Lecture 9

45



## Example: S/1

- Backtrace from r again

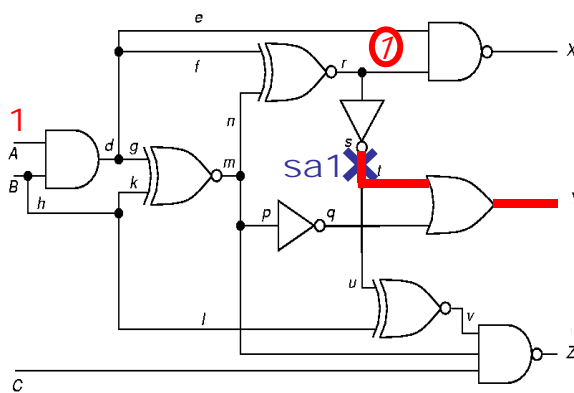

Copyright 2019, M. Tahoori

TDS I: Lecture 9

46

### Example: S/1

- Set  $B = 0$ .
- Implications in stack:  $A = 1, B = 0$

Copyright 2019, M. Tahoori TDS I: Lecture 9 47

### Example: S/1

- Forward implications:
  - $d = 0, X = 1, m = 1, r = 0$ .
- Conflict: fault not sensitized. Backtrack


Copyright 2019, M. Tahoori TDS I: Lecture 9 48





## Example: S/1

- Set B = 1 (alternative assignment)

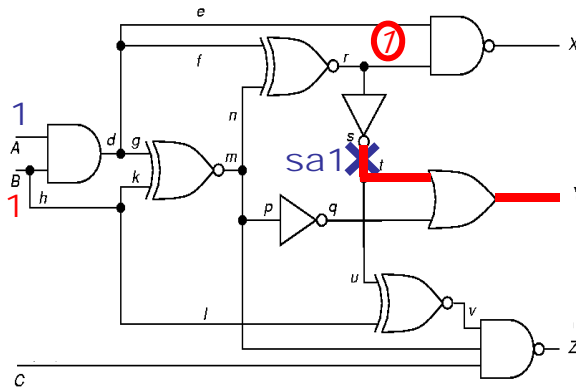

Copyright 2019, M. Tahoori


TDS I: Lecture 9

49


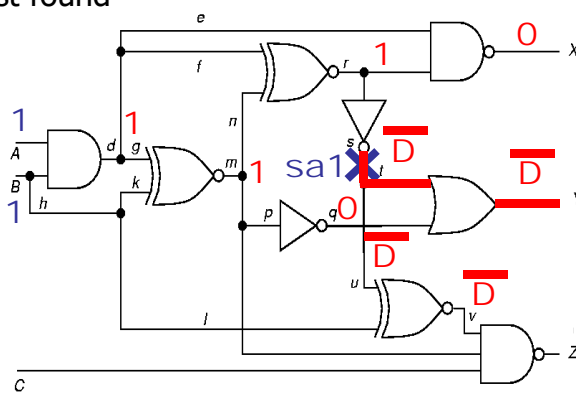
## Example: S/1


- Forward implications:
  - $d = 1, m = 1, r = 1, q = 0, s = \overline{D}, v = \overline{D}, X = 0, Y = \overline{D}$
- Test found



Copyright 2019, M. Tahoori

TDS I: Lecture 9


50



## PODEM

- Major aspects
  - Which primary input should be assigned a logic value?
  - What value to assign to the selected primary input?
  - Determining inconsistencies in primary input assignments
  - Handling inconsistencies

Copyright 2019, M. Tahoori TDS I: Lecture 9 51



## Which PI to Choose?

- Decision gate
  - Logic value at the output of a gate is such that only one input of the gate can control its output to the desired value
    - AND with output 0
- Imply gate
  - Logic value at the output of a gate is such that all inputs of the gate must be at a particular value in order to control its output to the desired value
    - AND with output 1
- To justify a logic value at the output of a decision gate, choose the "easiest" input.
  - The shortest logical path to primary inputs or has the best controllability
- To justify a logic value at the output of an imply gate, choose the "hardest" input
  - The longest logical path to primary inputs or has the worst controllability

Copyright 2019, M. Tahoori TDS I: Lecture 9 52



## What Value to Assign?

- Path from the objective site to the selected primary input has an **even** number of inversions
  - Assign the same value to PI as the objective
- Path from the objective site to the selected primary input has an **odd** number of inversions
  - Assign the opposite value of the objective to PI



## Inconsistencies in PI Assignment

- After every primary input assignment, an implication step is performed.
- During implication, inconsistencies in primary input assignments are detected using the following rules:
  - If there are conflicting assignments at the same signal line of the network
  - If the logic value at the fault site doesn't activate the fault
  - If there is no path from the fault site to a primary output such that all side inputs of that path are either X or set at non-controlling values



## Handling Inconsistencies

- Backtracking
  - Flip the logic value at the primary input
    - Which was the last one to be assigned a value
  - Stack of primary inputs that have been assigned values
  - After flipping implication step is performed
    - No inconsistency detected
      - Continue
    - Otherwise
      - That primary input is removed from the stack and
        - X is assigned to that primary input
      - POP the next assigned PI from stack and repeat