

# Testing Digital Systems II

# Lecture 5: Built-in Self Test (I)

Instructor: M. Tahoori

Copyright 2010, M. Tahoori

TDS II: Lecture 5

1



#### **Outline**

- Introduction (Lecture 5)
- Test Pattern Generation (Lecture 5)
  - Pseudo-Random
  - Pseudo-Exhaustive
- Output Response Analysis (Lecture 6)
  - Duplication
  - Response Compaction
    - Signature Analysis
- BIST Architectures (Lecture 7)

Copyright 2010, M. Tahoori

TDS II: Lecture 5

2



#### **Built-In Self Test**

- Definition:
  - Capability of a Product
    - chip, multichip assembly, or system
  - To carry out an explicit test of itself
- Requires
  - Test Pattern Generation
  - Output Response Analysis
  - One or both integral to the product
  - Minimal external test equipment required


Copyright 2010, M. Tahoori

TDS II: Lecture 5

3



# A Typical Logic BIST System

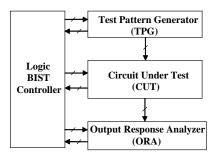

#### Structural off-line BIST

Copyright 2010, M. Tahoori

TDS II: Lecture 5



#### **Built-In Self Test**

- Why BIST (Built-In Self Test) ?
  - Improved product quality
  - Faster debug
  - Better diagnosis
  - Thorough test very many high-speed patterns
  - Economical production test
  - Improved field test and maintainability
- What are its drawbacks?
  - Initial design investment
  - Possible performance or area overhead

Copyright 2010, M. Tahoori

TDS II: Lecture 5

5



## **BIST Techniques**

- Enhanced functional self-test software routines
- Exhaustive and pseudo-exhaustive
- Pseudo-random (PR-BIST)

Copyright 2010, M. Tahoori

TDS II: Lecture 5

6



## **BIST Techniques**

- Enhanced functional self-test software routines
  - For field test and diagnosis
  - Advantage:
    - No hardware modifications
  - Disadvantages:
    - Low hardware fault coverage
    - Low diagnostic resolution
    - Slow to operate
    - Labor intensive, low fault coverage
- Exhaustive and pseudo-exhaustive
  - + Thorough test of stuck faults
  - + Minimal simulation required
  - Difficult to implement for arbitrary designs

Copyright 2010, M. Tahoori

TDS II: Lecture 5

7



### **BIST Techniques**

- Pseudo-Random (PR-BIST)
  - Separate (Serial Scan-Loaded Test Patterns)
    - External Pattern Generation, Response Analysis
  - Embedded PR-BIST (System Bistables Reconfigured)
    - BILBO Multiple Test Configurations
    - Circular

Copyright 2010, M. Tahoori

TDS II: Lecture 5

8



#### **BIST Attributes: Fault Characteristics**

- Fault classes tested
  - Single-stuck faults in functional circuitry
  - Combinational faults in functional circuitry
  - Delay faults
  - Interchip wiring and chip I/O connections
- Fault coverage
  - Percentage of faults guaranteed to be detected

Copyright 2010, M. Tahoori

TDS II: Lecture 5

9



## **BIST Attributes: Cost Characteristics**

- Area overhead
  - Additional active area, interconnect area
    - Test controller
    - Hardware pattern generator
    - Hardware response compacter
    - Testing of BIST hardware
- Pin overhead: Additional pins required for testing
- Performance penalty: Added path delays
- Yield loss: Due to increased area
- Reliability reduction: Due to increased area

Copyright 2010, M. Tahoori

TDS II: Lecture 5

10



### **BIST Attributes: Other Characteristics**

- Generality
  - Degree of function dependence
- Time required to execute test
- Diagnostic resolution
- Engineering changes
  - Effect on BIST structure
- Functional circuitry
  - Scan path?
  - Design changes?

Copyright 2010, M. Tahoori

TDS II: Lecture 5

11



# BIST Attributes: Other Characteristics

- Test Pattern Generation
  - Exhaustive
  - Pseudo-Exhaustive
  - Pseudo-Random
- Response Analysis
  - LFSR
  - Duplication

Copyright 2010, M. Tahoori

TDS II: Lecture 5

12



### **Exhaustive and Pseudo-Exhaustive Test**

- Exhaustive Test of n-Input Combinational Circuit
  - Apply all N = 2<sup>n</sup> Patterns
- Pseudo-Exhaustive Test of Combinational Circuit
  - Subdivide the Circuit into Segments
  - Apply all Possible Inputs to each Segment
- Input patterns 2<sup>m</sup> m-bit patterns
  - binary counter
  - Gray counter
  - m-stage Modified ALFSR

Copyright 2010, M. Tahoori

TDS II: Lecture 5

13



#### **Test Patterns**

- Stored Off Line
  - Patterns are generated and stored
  - Simulation used to identify patterns for removal
- "Just-in-Time"
  - Patterns are generated during test application
    - External tester generates patterns
    - Patterns generated on same chip or board as device under test
  - +Easy to Generate
  - +Detect Non- single-stuck faults
  - -Long
    - Coverage Expensive to Determine

Copyright 2010, M. Tahoori

TDS II: Lecture 5

14



## Random vs Pseudorandom

- Random Source
  - Patterns can occur more than once
  - Non-reproducible
- Pseudorandom Source
  - All (possibly except all-0 pattern) Patterns
    - Occur Before Any Pattern Repeats
  - Reproducible

Copyright 2010, M. Tahoori

TDS II: Lecture 5

15



### **Test Pattern Generator**

Copyright 2010, M. Tahoori


TDS II: Lecture 5

16


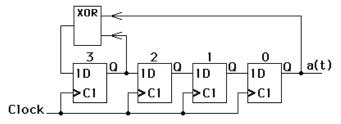
## Pseudo-Random Test Pattern Generator

- Four-stage ALFSR Standard or External Form
  - Autonomous Linear Feedback Shift Register



- Output Sequence:  $a(t + 4) = a(t + 3) \oplus a(t)$
- Generating Function:  $f(x) = x^4 + x^3 + 1$
- Feedback Vector:  $H = \langle h_4, h_3, ..., h_0 \rangle = \langle 1, 1, 0, 0, 1 \rangle$

Copyright 2010, M. Tahoori

TDS II: Lecture 5

17



# Pseudo-Random Test Pattern Generator

- Operator Notation
  - $X^i a(t) = a(t+i)$
  - $(X^3 + X + 1) a(t) = a(t+3) + a(t+1) + a(t)$


Copyright 2010, M. Tahoori

TDS II: Lecture 5

18



## Standard Form ALFSR

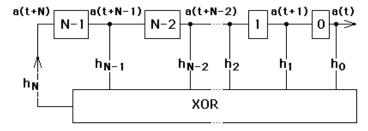

- Output Sequence:  $a(t+N) = \sum_{i=0}^{N-1} h_i a(t+i)$  Modulo 2
- Generating Function:  $f(x) = \sum_{i=0}^{N} h_i x^i$  Modulo 2


Copyright 2010, M. Tahoori

TDS II: Lecture 5

19



# Four-Stage Modular ALFSR (Divider)

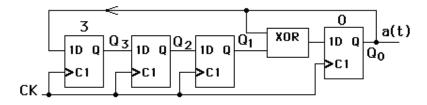

- Generating Function:  $f(x) = x^4 + x^3 + 1$
- Feedback Vector:  $H = \langle h_4, h_3, ..., h_0 \rangle = \langle 1, 1, 0, 0, 1 \rangle$


Copyright 2010, M. Tahoori


TDS II: Lecture 5


20


Lecture 5


10

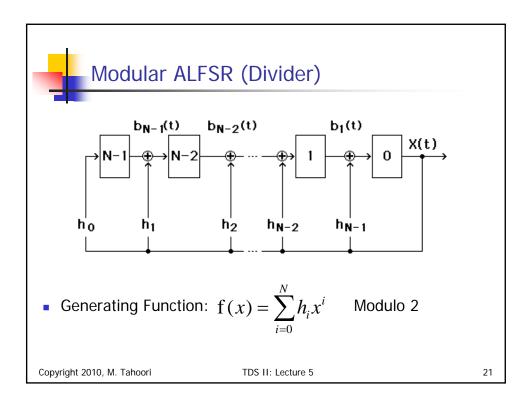


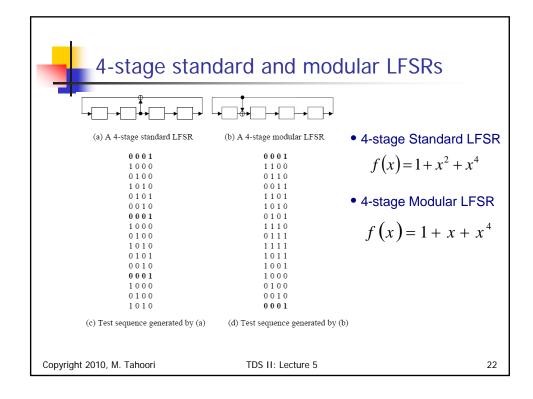

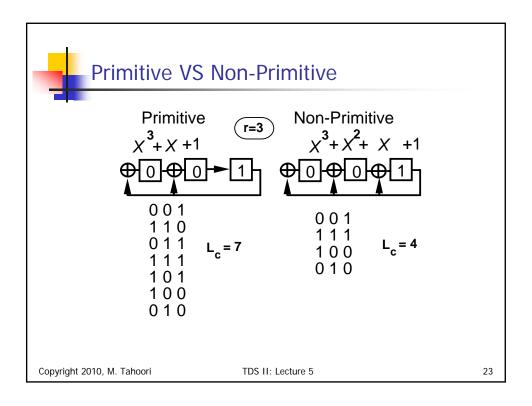

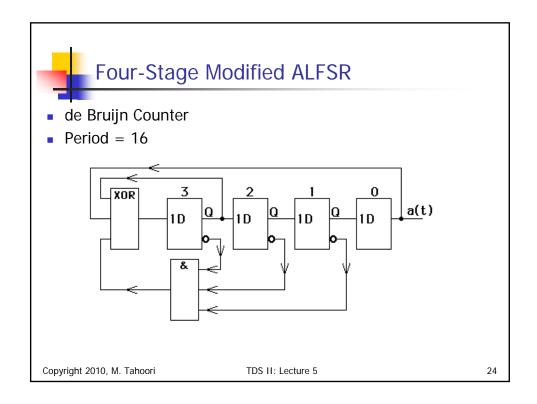

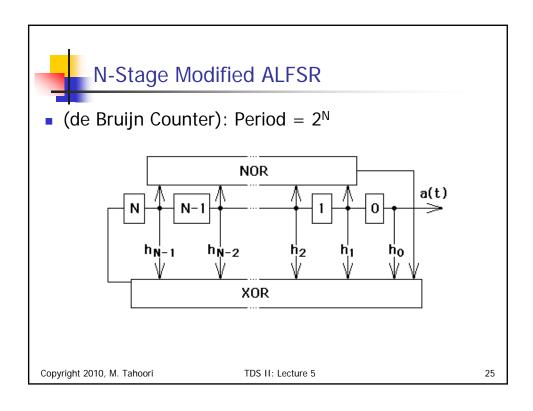

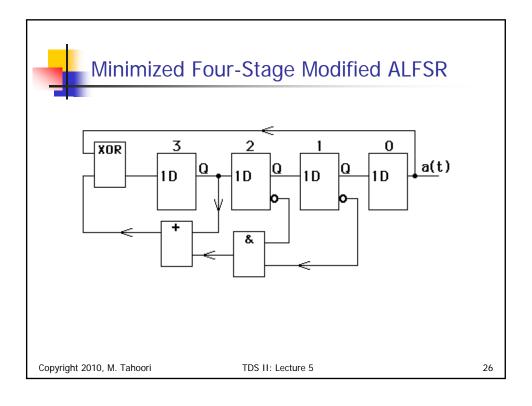



### Test Architecture

- m-stage ALFSR generates L m-bit patterns
  - L is test length
  - M = 2<sup>m</sup> 1 is number of patterns generated
- n is number of inputs for network under test (NUT)
  - N = 2<sup>n</sup> is exhaustive test length for NUT
    - Patterns generated on same chip or board
      - as device under test


Copyright 2010, M. Tahoori

TDS II: Lecture 5

27



## **Test Architecture**

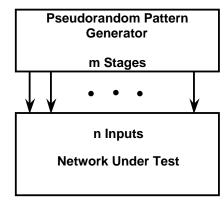

Copyright 2010, M. Tahoori

TDS II: Lecture 5

28