

Testing Digital Systems II

Lecture 7: Built-in Self Test (III)

Instructor: M. Tahoori

Copyright 2010, M. Tahoori TDS II: Lecture 7 1



BIST Architectures

Copyright 2010, M. Tahoori TDS II: Lecture 7 2

Logic BIST Architectures

Four Types of BIST Architectures:

- No special structure to the CUT
- Make use of scan chains in the CUT
- Configure the scan chains for test pattern generation and output response analysis
- Use concurrent checking circuitry of the design


Copyright 2010, M. Tahoori

TDS II: Lecture 7

3

Centralized and Separate Board-Level BIST (CSBL)

 - Two LFSRs and two multiplexers are added to the circuit.
- The first LFSR acts as a PRPG, the second serves as a SISR.
- The first multiplexer selects the inputs, another routes the PO to the SISR.



CSBL Architecture

[Benowitz 1975]


Copyright 2010, M. Tahoori

TDS II: Lecture 7

4

Built-In Evaluation and Self-Test (BEST)

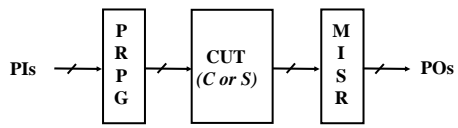- Use a PRPG and a MISR.
- Pseudo-random patterns are applied in parallel from the PRPG to the chip primary inputs (PIs)
- MISR is used to compact the chip output responses




BEST Architecture

[Perkins 1980]

Copyright 2010, M. Tahoori TDS II: Lecture 7 5

Separate PR-BIST

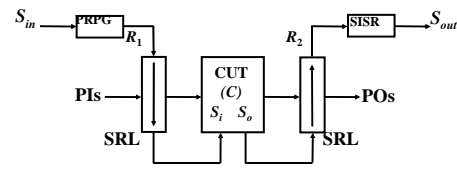- In addition to the internal scan chain, an external scan chain comprising all primary inputs and primary outputs is required.
- The External scan-chain input is connected to the scan-out point of the internal scan chain.



LOCST Architecture

[Eichelberger 1983]

Copyright 2010, M. Tahoori TDS II: Lecture 7 6

Separate PR-BIST

NORMAL
Shift Test Pattern In,
Response Out
Apply Pattern,
Get Response

- Drawbacks: Long Test Time, Poor Delay Fault Cover
- Advantages: Low Overhead, Simple Control Logic

Copyright 2010, M. Tahoori TDS II: Lecture 7 7

Test-per-Clock System

- New fault set tested every clock period
- Shortest possible pattern length
 - 10 million BIST vectors, 200 MHz test / clock
 - Test Time = $10,000,000 / 200 \times 10^6 = 0.05 \text{ s}$

Copyright 2010, M. Tahoori TDS II: Lecture 7 8



Test-per-Scan System

- New fault tested during 1 clock vector with a complete scan chain shift
- More time required per test than test-per-clock
 - Advantage:
 - Combination of scan chains and MISR reduces MISR bit width
 - Disadvantage:
 - Much longer test pattern set length, causes fault simulation problems
- Input patterns – time shifted & repeated
 - Become correlated – reduces fault detection effectiveness
 - Use XOR network to phase shift & decorrelate




STUMPS


- **Self-Test Using MISR and Parallel Shift register** sequence generator
- Originally proposed to reduce overhead of LFSR/MISR for application to testing multi-chip boards, each of which has only the Shift Registers
- Can also be used on a single chip with multiple scan chains

STUMPS Example

 - SR1 ... SRn – 25 full-scan chains, each 200 bits
- 5000 chip outputs, need 25 bit MISR (not 5000 bits)



STUMPS

 

A STUMPS-based Architecture

Copyright 2010, M. Tahoori

TDS II: Lecture 7

11

STUMPS

- Test procedure:
 - Scan in patterns from LFSR into all scan chains (200 clocks)
 - Switch to normal functional mode and clock 1 x with system clock
 - Scan out chains into MISR (200 clocks) where test results are compacted
 - Overlap Steps 1 & 3
- Requirements:
 - Every system input is driven by a scan chain
 - Every system output is caught in a scan chain or drives another chip being sampled

Copyright 2010, M. Tahoori

TDS II: Lecture 7

12

Built-In Logic Block Observer (BILBO)


- The architecture applies to circuits that can be partitioned into independent modules (logic blocks).
- Each module is assumed to have its own input and output registers (storage elements)
 - Or such registers are added to the circuit where necessary.
- The registers are redesigned so that for test purposes they act as PRPGs or MISRs.

Copyright 2010, M. Tahoori

TDS II: Lecture 7

13

Embedded PR-BIST —BILBO

 

- Drawbacks: Multiple Test Sessions, Complex Control
 - Register Self-adjacency Concerns
- Advantages: At-speed Test, Reuse System Bistables

Copyright 2010, M. Tahoori

TDS II: Lecture 7

14

Built-In Logic Block Observer

B ₁	B ₂	Operation mode
1	1	Normal
0	0	Scan
1	0	Mixed Test Generation and Signature Analysis
0	1	Reset

A 3-stage BILBO

Copyright 2010, M. Tahoori TDS II: Lecture 7 15

Another BILBO Register

- B1 and B2 configure as
 - **Shift register** for scan (B1B2= 00),
 - **LFSR** (B1B2 = 01),
 - **MISR** (B1B2 = 11)
 - **Normal** (B1B2 = 10)

Copyright 2010, M. Tahoori TDS II: Lecture 7 16

Example BILBO Usage

- SI – Scan In
- SO – Scan Out
- Characteristic polynomial: $1 + x + \dots + x^n$
- CUTs A and C: BILBO1 is MISR, BILBO2 is LFSR
- CUT B: BILBO1 is LFSR, BILBO2 is MISR

(a) Example test configuration.


Copyright 2010, M. Tahoori TDS II: Lecture 7 17

Register self-Adjacency


- Register $R2$ is self-adjacent
 - It should act as LFSR and MISR at the same time
 - Cannot use BILBO register

Copyright 2010, M. Tahoori TDS II: Lecture 7 18

Embedded PR-BIST —Circular

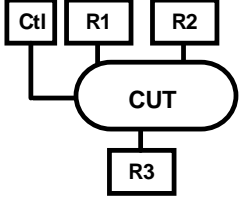

Normal

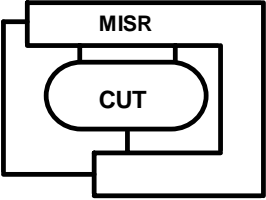


Test

- Drawbacks: Scan Dependence Concerns
- Advantages: At-speed Test, Reuse System Bistables
 - Simple Control Logic, Short Test Time

Copyright 2010, M. Tahoori TDS II: Lecture 7 19

Concurrent Built-In Logic Block Observer (CBILBO)

B ₁	B ₂	Operation mode
-	0	Normal
1	1	Scan
0	1	Test Generation and Signature Analysis

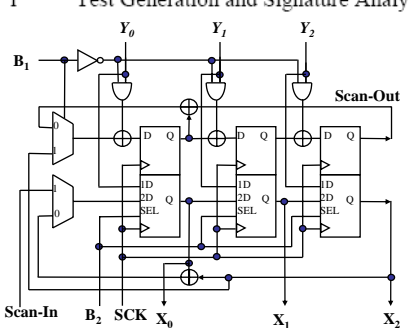

[Wang 1986c]

A 3-stage concurrent BILBO (CBILBO)

Copyright 2010, M. Tahoori TDS II: Lecture 7 20

Circular Self-Test Path

(a) The CSTP architecture
(b) Self-Test cell

CSTP architecture

Copyright 2010, M. Tahoori TDS II: Lecture 7 21

Concurrent Self-Verification (CSV)

CSV Architecture

Copyright 2010, M. Tahoori TDS II: Lecture 7 22



Summary

<i>Architecture</i>	<i>Level</i>	<i>TPG</i>	<i>ORA</i>	<i>Circuit</i>	<i>BIST</i>
CSBL	B or C	PRPG	SISR	C or S	Test-Per-Clock
BEST	B or C	PRPG	MISR	C or S	Test-Per-Clock
LOCST	C	PRPG	SISR	C	Test-Per-Scan
STUMPS	B or C	PRPG	MISR	C	Test-Per-Scan
BILBO	C	PRPG	MISR	C	Test-Per-Clock
CBILBO	C	EPG/PEPG	MISR	C	Test-Per-Clock
CSTP	C	PRPG	MISR	C or S	Test-Per-Clock
CSV	C	PRPG	Checker	C or S	Test-Per-Clock

B: board-level testing

C: combinational circuit

S: sequential circuit

Representative Logic BIST Architectures